

Architecture Lab 3 Report

2) A technical summary of experiments conducted in the lab (steps, results, components, code functionality, etc.)

- **Experiment 1:**

This experiment aims to implement an N-bit register with reset and load control

- In order to implement such a circuit, we should do the following:
 - 1- Create three module: DFlipFlop, MUX_2_to_1, n_bit_register
 - 2- DFlipFlop module acts as a single bit register that saves its value until D changes from Q in any positive clock edge
 - 3- MUX_2_to_1 module selects which value will enter the flipflop from D depending on the selector of the MUX.
 - 4- n_bit_register module assembles all the muxes and flipflops to act as one block that can store n bits and have a reset input which if it was high, all the flipflops will reset to zero.

For example:

In this block of code, we generate n 2 by 1 muxes and n DFlipFlops that all together act as an n bit register

```
generate
  for(i=0;i<n;i=i+1)
    begin:RegUnit
      MUX_2_to_1 mux(.A(Q[i]),.B(D[i]),.select(load),.C(C[i]));
      DFlipFlop flipflop(.clk(clk),.rst(reset),.D(C[i]),.Q(Q[i]));
    end
endgenerate
```

- **Experiment 2:**

This experiment aims to implement an n-bit 2x1 multiplexer which chooses between two n-bit inputs according to the input selector

- In order to implement such a circuit, we should do the following:
 - 1- Create two module: TwoByOneMux, nbitMux
 - 2- TwoByOneMux module is a normal 2 by 1 mux that selects one of two inputs depending on the input selector.
 - 3- nbitMux module which instantiates TwoByOneMux module n times in order to choose between the two n-input bits and will output either one of them depending on the selector.

For example:

```
generate for(i=0;i<N;i=i+1)
  TwoByOneMux m(a[i],b[i],s,c[i]); // we just generate n two by one muxes in order to
                                     //choose only one input from the two n-bits input
endgenerate
```

- **Experiment 3:**

This experiment aims to implement a circuit which shifts the bits to the left by 1 place

- In order to implement such a circuit, we should do the following:

1- Create one module: A n-bit shift left 1 module.

2- This n-bit shift left 1 module is nothing but a rewiring for the n-bits input, where we connect the least significant bit (i.e. number 0) to bit number 1 (the wire on the left), and so on until we leave one disconnected wire which is the left-most (most significant) bit. Besides, we connect the least significant bit of the other bus to the ground.

For example:

```
always @(*)
  begin
    for(i=1;i<=31;i=i+1)
      begin
        ShiftOut2[i]=In_Shift[i-1]; //here, we rewire each input to the wire right to the left to it
      end
    ShiftOut2[0]=1'b0; // then we connect the right most output wire to the ground since it
                        //has no input
  end
```

- **Experiment 4:**

This experiment aims to implement a circuit which generates and reassembles the immediate bits that are found in the types of different instructions and then extends the sign on the most significant bit in the immediate bus

- In order to implement such a circuit, we should do the following:

1- Create one module: an ImmGen module.

2- This module assembles the scattered immediate bits in the different instructions depending on the instruction itself.

For example:

```
if(inst[6]) begin // in case of BEQ instruction
  gen_out[11]=inst[31];
  gen_out[10]=inst[7]; // a concatenation of bits 31, 7, 30:25, and 11:8 for BEQ
```

```

    gen_out[9:4]=inst[30:25];
    gen_out[3:0]=inst[11:8];
    gen_out[31:12]={20{gen_out[11]}};
end
else if(inst[5]) begin          // in case of SW instruction
    gen_out[11:5]=inst[31:25];
    gen_out[4:0]=inst[11:7];    // a concatenation of bits 31:25 and 11:7 for SW
    gen_out[31:12]={20{gen_out[11]}};
end
else begin                    // in case of LW instruction
    gen_out[11:0]=inst[31:20]; // bits 31:20 for LW
    gen_out[31:12]={20{gen_out[11]}};
end
end

```

3) Verilog code for all modules of each experiment.


- Verilog code of each experiment is attached in the zip file

4) Verilog code for the testbench module of each experiment's top-level module.

- Verilog code for the testbench is attached in the zip file


5) Snapshot of simulation output:

- **EXP1 Simulation Snapshot:**

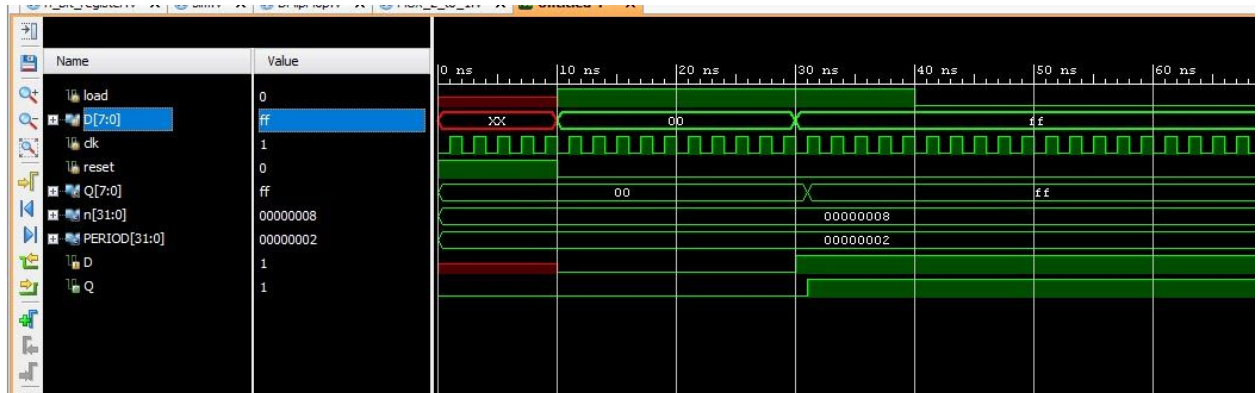

Here, we can see that when:

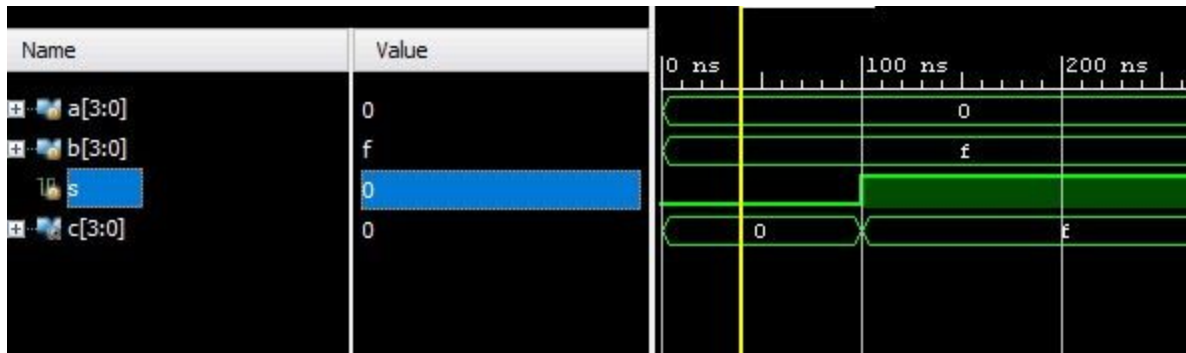
- Reset = 0 → Q=8'b00000000
 - reset=0 & D=8'b00000000 & load=1 → Q=8'b00000000
 - D=8'b00000000 & load=1 → Q=8'b00000000
 - D=8'b11111111 & load=1 → Q=8'b11111111 (after the first positive clock edge)
 - D=8'b11111111 & load=0 → Q=(last Q)= 8'b11111111
- **EXP2 Simulation Snapshot:**



Here, we can see that when:

- $a=4'b0000$ & $b=4'b1111$ & $s=1'b0 \rightarrow$ since selection =0 so the output $c=4'b0000$
- $s=1'b1 \rightarrow$ since selection =1 so the output equal to the second input $c=4'b1111$


- EXP3 Simulation Snapshot:

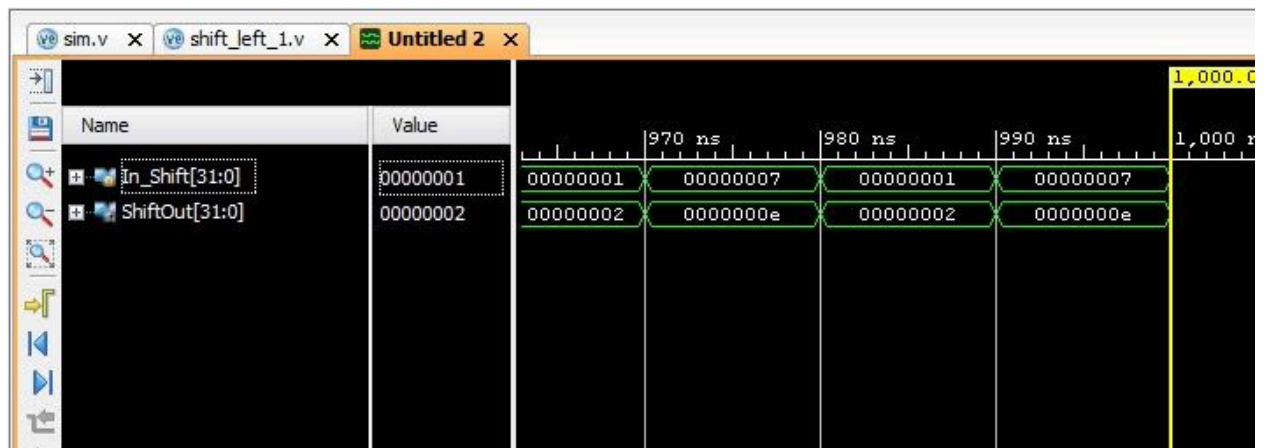

Here, we can see that when:

- $In_Shift=32'b00000000000000000000000000000001$ (1 in decimal) \rightarrow
 $ShiftOut=32'b00000000000000000000000000000010$ (2 in decimal)
- $In_Shift=32'b00000000000000000000000000000111$ (7 in decimal) \rightarrow
 $ShiftOut=32'b00000000000000000000000000001110$ (14 in decimal= e in hexa)

- EXP4 Simulation Snapshot:

 

Here, we can see that when:

- $i=32'b010011010110_00101_010_00110_0000011$ (LW) \rightarrow 1238
- $i=32'b1101110_01010_01111_010_11110_0100011$ (SW) \rightarrow -546
- $i=32'b0001100_01110_00011_000_11110_1100011$ (BEQ) \rightarrow 207

6) Schematic design to our N-Bit register to allow extra input Shift:

- If (shift control==1 && load==0) shifts the data in the register 1 bit to the left.
- If (shift control==1 && load==1) load data ignore shifting

