

**Architecture Lab 2 Report**

**Experiment 0:**

- This experiment aims to use the UART module as the input to the board instead of the switches. This can be done by sending serial commands to the module through a terminal program which will convert it to a signal that will be used as our input in the future experiments.

**Experiment 1:**

- This experiment aims to implement a 4-bit ripple carry adder (RCA) which takes two 4-bit input positive numbers and returns their sum as an output.
- In order to implement such a circuit, we should do the following:

1- write a "Full\_Adder" module that adds two bits and acts as the building block of the ripple carry adder.

2- write an "RCA4" module that instantiates  $n$  instances of the Full\_Adder module

3- Add the modules used in lab1 to this experiment in order to be able to see the results of the experiment on the 7-segment display.

4- write a "const" file in order to inform the software what physical pins on the Nexys A7-100T FPGA Board that we plan on using or connecting to in relation to the Verilog code that we wrote to describe the behavior of the FPGA.

- **Explaining code functionality by commenting on the code:**

```
module Full_Adder(           // the full adder module takes three inputs: two bits and a
                             // carry in if exists and outputs the sum of these two bits
                             // and a carry out if exists (i.e. 1 bit + 1 bit = 0 bit + carryout)
    input x,y,cin,
    output sum,carry_out
);
    assign sum = x ^ y ^ cin; // the sum can be computed by xoring the three inputs
    assign carry_out = x&y | (x^y) & cin;
```

Endmodule

```
module RCA4 #(parameter n = 4) (input [n-1:0] x,input [n-1:0] y,input cin, output [n:0]
out,output last_carry);
```

// The ripple carry adder module takes 3 inputs: 2 4-bits input numbers and a carry-in if exists and outputs the sum of these two numbers and the last carry if exists.

```
wire [n-1:0] sum;
wire carry[n:0]; // this bus of wires is used to store all the carry-ins
assign carry[0]=cin;
```

```
genvar i;
Generate // generate block to instantiate the full adder module n times
for(i=0;i<n;i=i+1)
begin
Full_Adder fa(.x(x[i]),.y(y[i]),.cin(carry[i]),.sum(sum[i]),.carry_out(carry[i+1]));
end
endgenerate
```


```
assign out={carry[n],sum};
```

```
assign last_carry=carry[n];
```


endmodule

## Schematics:

With the UART module:

 

Without the UART module:

 

It would be apparent that this implementation is simpler than the circuit found in experiment three which will eventually result in the longer delay.

### Utilization Hierarchy:

Name	^1	Slice LUTs (63400)	Slice Registers (126800)	Slice (15850)	LUT as Logic (63400)	LUT Flip Flop Pairs (63400)	Bonded IOB (210)	BUFGCTRL (32)
Four_Digit_Seven_Segment_Dr...		226	316	122	226	100	13	1
no_label_line35 (UART_recei...		223	296	117	223	99	0	0

### Utilization Report:

1. Slice Logic					
Site Type	Used	Fixed	Available	Util%	
Slice LUTs	226	0	63400	0.36	
LUT as Logic	226	0	63400	0.36	
LUT as Memory	0	0	19000	0.00	
Slice Registers	316	0	126800	0.25	
Register as Flip Flop	316	0	126800	0.25	
Register as Latch	0	0	126800	0.00	
F7 Muxes	0	0	31700	0.00	
F8 Muxes	0	0	15850	0.00	

Total slice LUTs used = 226

Total slice Registers used = 316

### Hold time:

Name	... ^1	Levels	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 31	∞	2		7 ref.../C	Anode[1]	2.103	1.445	0.657	-∞ sys_clk_pin	
Path 32	∞	3		7 ref.../C	LED_out[4]	2.152	1.448	0.704	-∞ sys_clk_pin	
Path 33	∞	2		7 ref.../C	Anode[0]	2.177	1.504	0.673	-∞ sys_clk_pin	
Path 34	∞	2		7 ref.../C	Anode[3]	2.272	1.521	0.752	-∞ sys_clk_pin	
Path 35	∞	3		7 ref.../C	LED_out[0]	2.362	1.492	0.870	-∞ sys_clk_pin	
Path 36	∞	3		7 ref.../C	LED_out[3]	2.388	1.505	0.883	-∞ sys_clk_pin	
Path 37	∞	2		7 ref.../C	Anode[2]	2.689	1.484	1.205	-∞ sys_clk_pin	

Hold time= 2.689

### Setup time:


Name	...	Levels	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 21	∞	4		7 nol.../C	LED_out[5]	10.930	4.383	6.547	∞ sys_clk_pin	
Path 22	∞	4		7 nol.../C	LED_out[6]	10.750	4.405	6.345	∞ sys_clk_pin	
Path 23	∞	4		7 nol.../C	LED_out[1]	10.173	4.389	5.784	∞ sys_clk_pin	
Path 24	∞	4		7 nol.../C	LED_out[2]	9.723	4.362	5.361	∞ sys_clk_pin	
Path 25	∞	4		7 nol.../C	LED_out[3]	9.625	4.378	5.247	∞ sys_clk_pin	
Path 26	∞	4		7 nol.../C	LED_out[0]	9.234	4.365	4.868	∞ sys_clk_pin	
Path 27	∞	4		7 nol.../C	LED_out[4]	9.018	4.321	4.697	∞ sys_clk_pin	

Setup time = 10.930

### Results

- As a result of this experiment, we can now press of the keyboard from home the two input 4-bits numbers and see the addition of them on the board.  
(as shown in the screenshot below)

### Camera Screenshot:

 

This screenshot shows the result of adding those two numbers in bits :

5 → 0101

2 → 0010

---

7 → 0111

### Experiment 2:

- This experiment aims to implement A 4-digit 7-segment display that takes a number and outputs it on the 4-digit 7-segment display.

- In order to implement such a circuit, we should do the following:
  - 1- Copy the code found in the first lap with optimization that displays the numbers on the 7-segment display.
  - 2- add on it a piece of code that detects the negative number and displays it on the screen .
  - 3- write an “FDSSD\_constraint” file in order to inform the software what physical pins on the Nexys A7-100T FPGA Board that we plan on using or connecting to in relation to the Verilog code that we wrote to describe the behavior of the FPGA.
- **Explaining code functionality by commenting on the code:**

```

reg [12:0] New_Num;
reg Sign;
integer i;
always @(*)
begin
  case(Num[7]) //We had to add this code that recognizes whether the input is negative or
              //not and if negative, it sets the sign register to 1 else it is 0.
    1'b0: begin
      Sign=1'b0;
      New_Num=Num;
    end
    1'b1: begin
      Sign=1'b1;
      New_Num=-Num; // if the numebr was negative we perform two's complement on it,
                  //where the two's complement of the negative number= positive
                  // number
    end
  endcase
end

```

### **Schematics:**

With the UART module:

**Hold time:**



Name	...	Levels	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 31	∞	2		13 ref.../C	Anode[1]	2.012	1.422	0.589	-∞ sys_clk_pin	
Path 32	∞	2		13 ref.../C	Anode[0]	2.059	1.422	0.637	-∞ sys_clk_pin	
Path 33	∞	2		13 ref.../C	Anode[3]	2.208	1.504	0.704	-∞ sys_clk_pin	
Path 34	∞	3		6 nol.../C	LED_out[4]	2.365	1.448	0.917	-∞ sys_clk_pin	
Path 35	∞	3		13 ref.../C	LED_out[0]	2.396	1.469	0.927	-∞ sys_clk_pin	
Path 36	∞	3		13 ref.../C	LED_out[3]	2.415	1.547	0.868	-∞ sys_clk_pin	
Path 37	∞	3		6 nol.../C	LED_out[2]	2.529	1.488	1.040	-∞ sys_clk_pin	


Hold time= 2.529

### Setup time:

Name	...	Levels	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 21	∞	5		9 nol.../C	LED_out[5]	11.624	4.569	7.054	∞ sys_clk_pin	
Path 22	∞	5		8 nol.../C	LED_out[1]	11.468	4.811	6.657	∞ sys_clk_pin	
Path 23	∞	5		8 nol.../C	LED_out[6]	11.352	4.591	6.761	∞ sys_clk_pin	
Path 24	∞	5		9 nol.../C	LED_out[2]	10.420	4.548	5.872	∞ sys_clk_pin	
Path 25	∞	5		8 nol.../C	LED_out[3]	10.177	4.794	5.383	∞ sys_clk_pin	
Path 26	∞	5		8 nol.../C	LED_out[0]	10.080	4.551	5.528	∞ sys_clk_pin	
Path 27	∞	5		8 nol.../C	LED_out[4]	9.844	4.507	5.337	∞ sys_clk_pin	

Setup time = 11.624

### Camera Screenshot:

 

This screenshot shows the result of entering a negative number 7:  
1001 → -7

### Experiment 3:


- This experiment aims to make a circuit that has two 4 bits input signed numbers and it adds them and displays the result on the 4 7-segment display with the negative sign if the number is negative.

## Explaining code functionality:


In this experiments' verilog code, we combined the code in the first experiemnt which is the 4 bits ripple carry adder and the code found in the second experiemnt which is the negative sign detection and conversion of the negative numbers to positive.

## Schematic:

With the UART module:

 

Without the UART module:

 

Here, it can be clearly seen that there are more components in the implementation of this circuit than the circuit found in experiment 1, since we added another logic for recognizing a negative number and displaying the negative sign on the first 7-segment display.

## Utilization Hierarchy:

Name	Slice LUTs (63400)	Slice Registers (126800)	Slice (15850)	LUT as Logic (63400)	LUT Flip Flop Pairs (63400)	Bonded IOB (210)	BUFGCTRL (32)
Four_Digit_Seven_Segment_Dr...	197	316	117	197	103	21	1
notabel_line36 (UART_recei...	194	296	111	194	102	0	0

## Utilization Report:



Site Type	Used	Fixed	Available	Util%
Slice LUTs	197	0	63400	0.31
LUT as Logic	197	0	63400	0.31
LUT as Memory	0	0	19000	0.00
Slice Registers	316	0	126800	0.25
Register as Flip Flop	316	0	126800	0.25
Register as Latch	0	0	126800	0.00
F7 Muxes	0	0	31700	0.00
F8 Muxes	0	0	15850	0.00

Total slice LUTs used = 197

Total slice Registers used = 316

### Hold time:

Name	...	Levels	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 31	∞	1		10 nol.../C	outp[4]	1.851	1.393	0.458	-∞ sys_clk_pin	
Path 32	∞	1		5 nol.../C	outp[3]	1.854	1.392	0.462	-∞ sys_clk_pin	
Path 33	∞	1		7 nol.../C	outp[1]	1.855	1.400	0.455	-∞ sys_clk_pin	
Path 34	∞	1		5 nol.../C	outp[2]	1.908	1.394	0.514	-∞ sys_clk_pin	
Path 35	∞	1		5 nol.../C	outp[6]	1.947	1.397	0.550	-∞ sys_clk_pin	
Path 36	∞	1		5 nol.../C	outp[7]	2.048	1.397	0.651	-∞ sys_clk_pin	
Path 37	∞	2		10 nol.../C	LED_out[4]	2.064	1.403	0.660	-∞ sys_clk_pin	


Hold time= 2.064

### Setup time:

Name	...	Levels	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 21	∞	4		13 ref.../C	LED_out[5]	11.086	4.611	6.475	∞ sys_clk_pin	
Path 22	∞	4		13 ref.../C	LED_out[6]	10.821	4.633	6.188	∞ sys_clk_pin	
Path 23	∞	4		13 ref.../C	LED_out[3]	10.714	4.606	6.108	∞ sys_clk_pin	
Path 24	∞	4		13 ref.../C	LED_out[1]	10.527	4.617	5.910	∞ sys_clk_pin	
Path 25	∞	4		13 ref.../C	LED_out[4]	10.216	4.549	5.667	∞ sys_clk_pin	
Path 26	∞	4		13 ref.../C	LED_out[2]	10.080	4.590	5.490	∞ sys_clk_pin	
Path 27	∞	2		13 ref.../C	Anode[2]	8.937	4.154	4.783	∞ sys_clk_pin	

Setup time = 11.086

### Camera Screenshot:

 

This screenshot shows the result of adding those two numbers in bits :

-5 → 1011

-2 → 1110

---

-7 → 1001

---

## Conclusion

	<u>Not optimized divisor (Experiment 1)</u>	<u>Optimized divisor (Experiment 3)</u>
Total slice LUTs used	226	197
Total slice Registers used	316	316
Hold time	2.689	2.064
Setup time	10.930	11.086

The circuit in experiment 3 clearly takes more setup time since it uses extra circuit components that are used to differentiate between a negative number and a positive number, and if the number is negative it performs two's complement on it in order to be seen as a positive number on the right with a negative sign on the left-most 7-segment displayer.